

K

Activity

Chat

Teams

Assignments

Calendar








Calls

Files

...

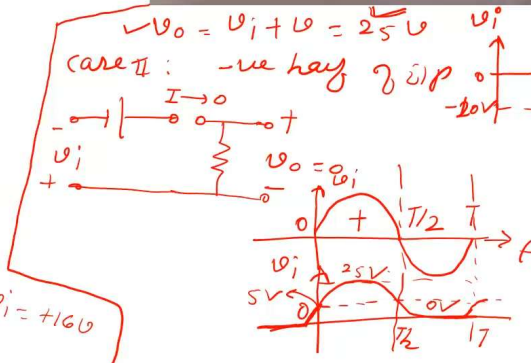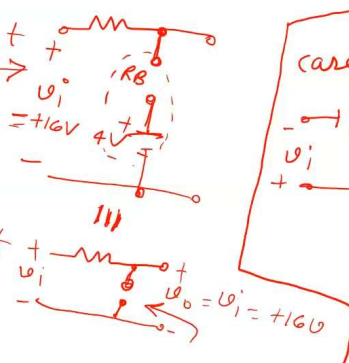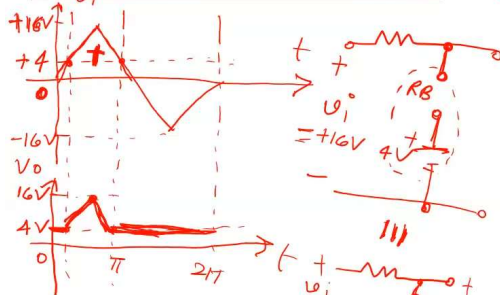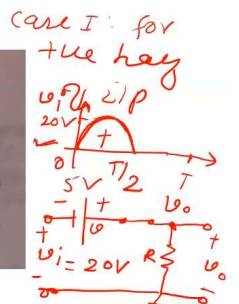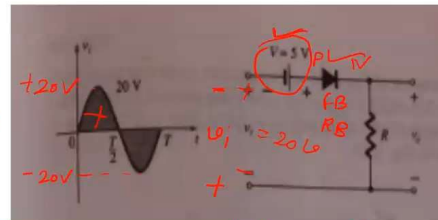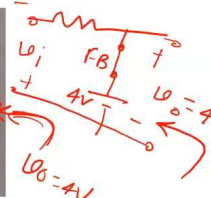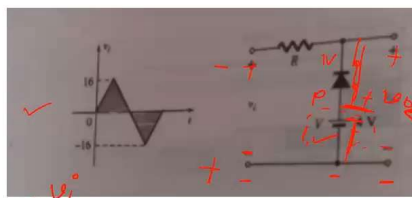Problem 4:

For the following Figures, determine the output voltage and sketch its nature



Apps

Help

57:48

L4 ECED ECED

