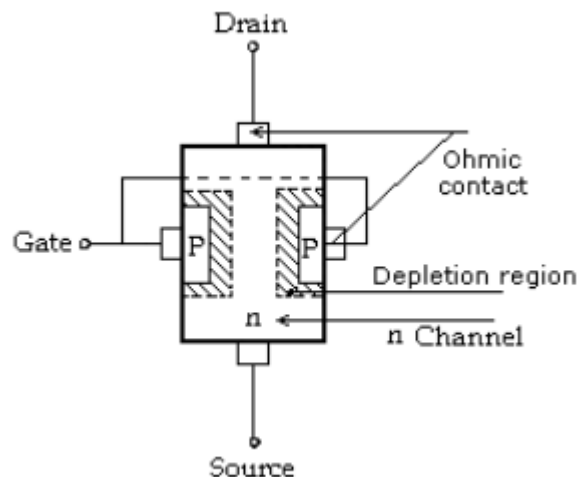


AIM: To study output and transfer characteristics of an n-channel Junction field effect Transistor (JFET) Amplifier

APPARATUS: JFET (BFW-10), Resistor (1K Ω , 100K Ω), Multisim Software.


Theory:



The basic construction of n-channel FET is as shown in figure. The major part of JEET is the channel between embedded P types of material. The top of the n-channel is connected to an ohmic contact called as 'Drain' (D) & lower end of Channel is called as 'Source' (S). The two p types of materials are connected together & to the 'Gate' terminal (G).

Characteristic:-

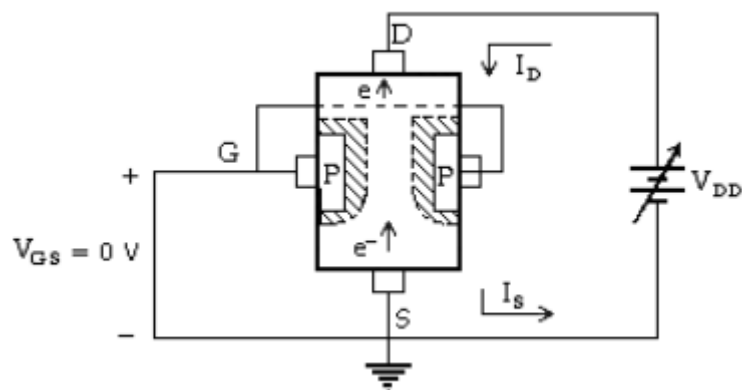
1. $V_{GS} = 0V$, V_{DS} - Some +ve Value:-




As shown in the figure the gate is directly connected to source to achieve $V_{GS} = 0V$, this is similar to no bias condition. The instant the voltage $V_{DD} (=V_{DS})$ is applied, the electrons will be drawn to the drain terminal, causing I_D & I_S to flow (i.e. $I_D = I_S$). Under this condition the flow of charge is limited solely by resistance of the n channel between drain & source. It is important to note that the depletion region wider at the top of both p type of material. Since the upper terminal is more R.B. than the lower terminal (source - S). As voltage V_{DS} is increased from 0 to few volts, the current will increase as determined by ohm's law. If still V_{DS} is increased & approaches a level referred as V_P , the depletion region will widen, causing a noticeable reduction in channel width. The reduced path of conduction causes the resistance to increase. The more the horizontal curve, the higher resistance. If V_{DS} is increase to a level where it appears that the two depletion region would touch each other, the condition referred as 'pinch-off' will result. The level of V_{DS} that establish this condition is called as 'pinch off voltage' (V_P). At V_P , I_D should be zero, but practically a small channel still exists & very high density current still flows through the channel. As V_{DS} is increased beyond V_P , the saturation current will flow through the channel (i.e I_{DSS}). I_{DSS} – Drain to source current with short cut connection from source to Gate.

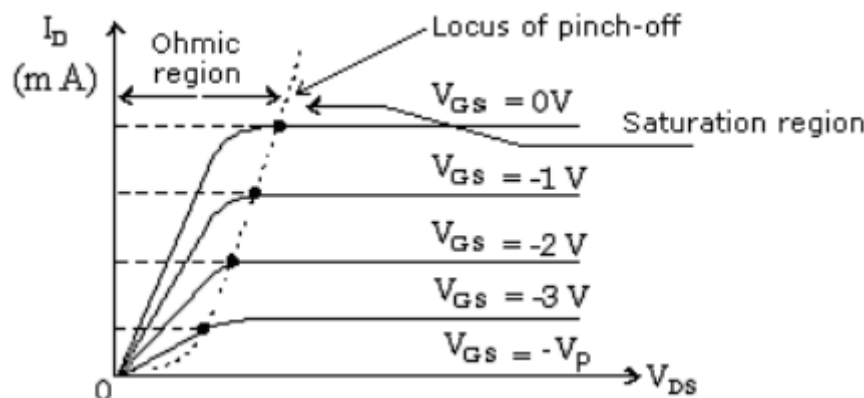2. $V_{GS} < 0V$:-

If a -ve bias is applied between gate and source, the effect of the applied -ve bias V_{GS} is to establish depletion region similar to those obtained with $V_{GS} = 0V$ but at lower level of V_{DS} . As V_{GS} will become more & more -ve biased, the depletion layer pinch off occur at the less & less value of V_{DS} . Eventually, when $V_{GS} = -V_P$, will be sufficiently -ve to establish a saturation level, i.e. essentially 0 mA & for all practical purpose the device has been 'turned OFF'



CIRCUIT DIAGRAM:

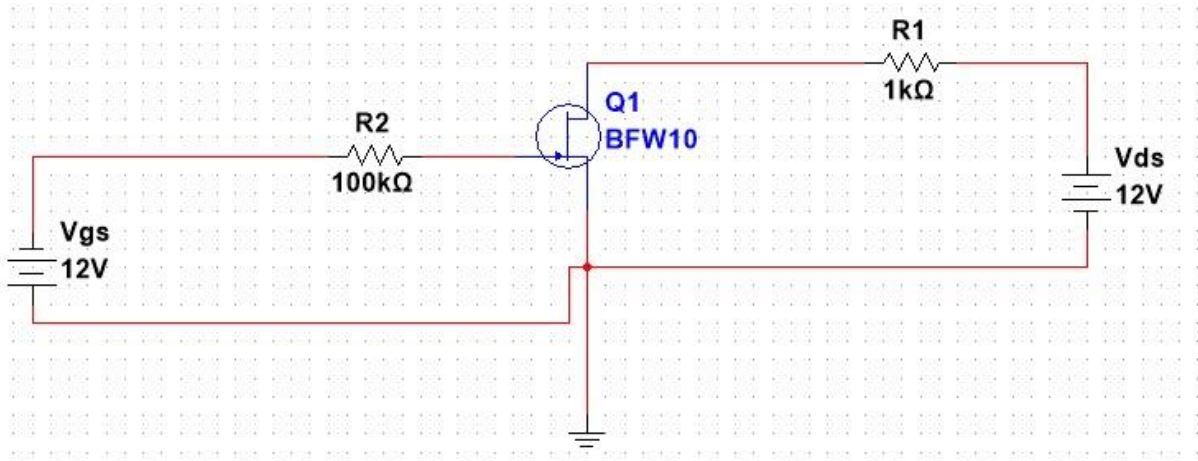

PROCEDURE:

OUTPUT CHARACTERISTICS:

1. Connect the circuit as per given diagram properly.
2. Keep $V_{GS} = 0V$
3. Vary V_{DS} in step of 0.5V up to 10 volts and measure the drain current I_D . Tabulate all the readings.
5. Repeat the above procedure for V_{GS} as -0.5, -1V, -1.5V, -2V.

TRANSFER CHARACTERISTICS:

1. Connect the circuit as per given diagram properly.
2. Keep V_{DS} constant at 2V.
3. Plot the transfer characteristics V_{GS} vs. I_D .
4. Repeat the above procedure for V_{DS} as 3, 4V.

Observation Table:**OUTPUT CHARACTERISTICS**

V _{gs} = 0V		V _{gs} = -0.5 V		V _{gs} = -1 V		V _{gs} = -1.5Vupto 2V	
V _{ds} (V)	I _d (mA)						
0							
1							
10							

Transfer Characteristics

V _{ds} (2V)		V _{ds} (3V)		V _{ds} (4V)	
V _{gs} (V)	I _d (mA)				
0					
-0.2					
-0.4					
-2					

CALCULATION:

1. Transconductance g_m : Ratio of small change in drain current (ΔI_D) to the corresponding change in gate to source voltage (ΔV_{GS}) for a constant V_{DS} .


$$g_m = \Delta I_D / \Delta V_{GS} \text{ at constant } V_{DS}$$

2. Output resistance: It is given by the relation of small change in drain to source voltage (ΔV_{DS}) to the corresponding change in Drain Current (ΔI_D) for a constant V_{GS} , when the JFET is operating in pinch-off region.


$$r_d \text{ or } r_o = \Delta V_{DS} / \Delta I_D \text{ at a constant } V_{GS}$$

Result:

OUTPUT CHARACTERISTICS

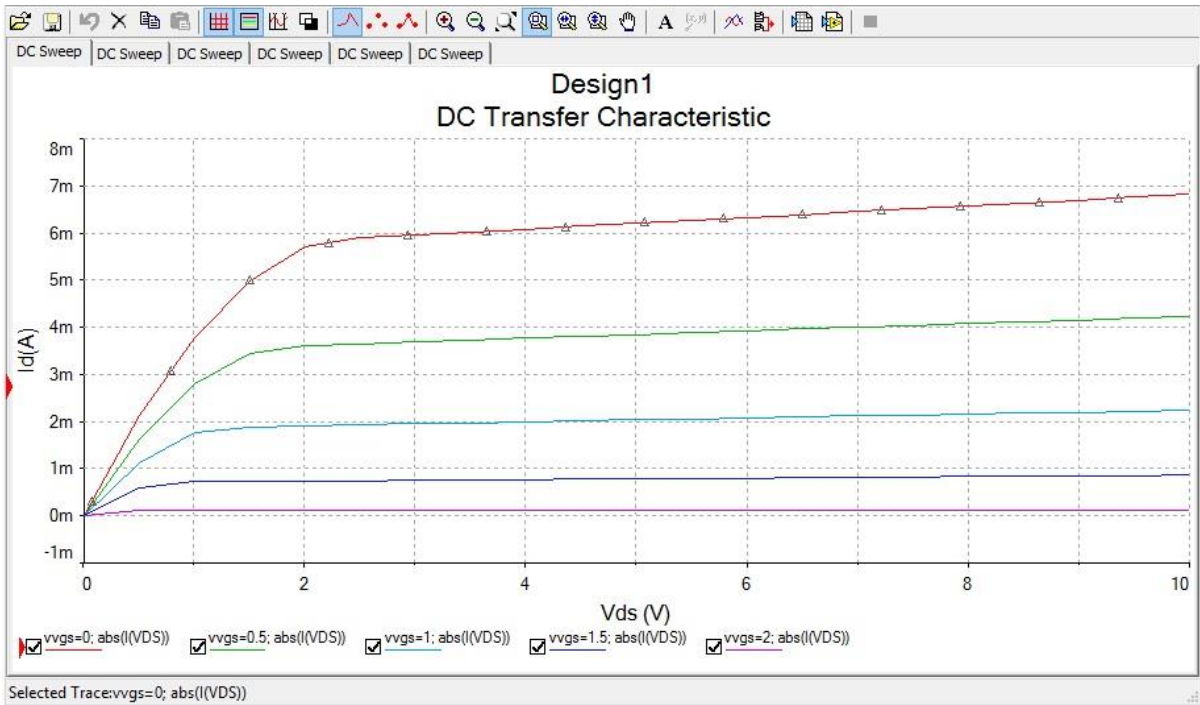

TRANSFER CHARACTERISTICS

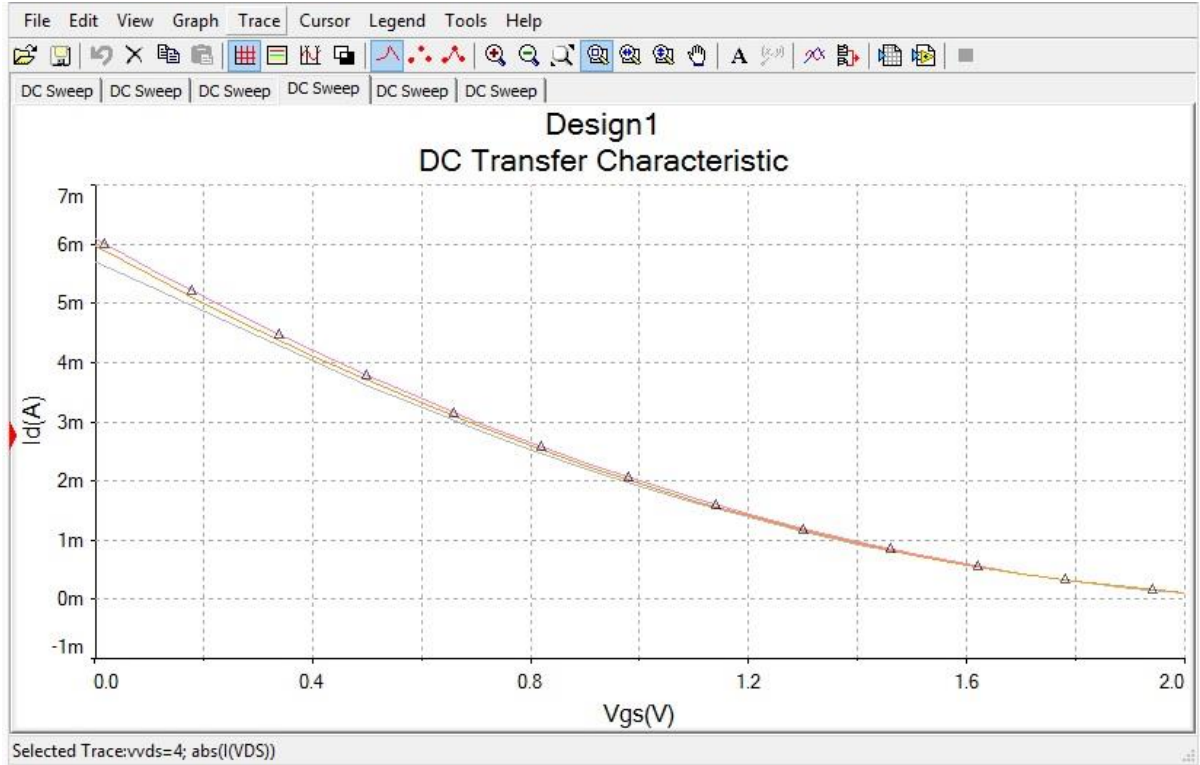

Conclusion: