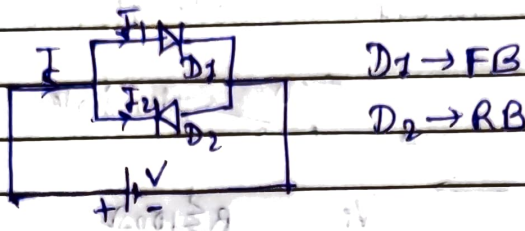


- (7) In the circuit below, the current voltage relationship when D_1 and D_2 are identical is given by (assume germanium diodes)



→ std diode current eqn is:

$$I = I_0 (e^{V_D/V_T} - 1) \quad \text{--- (7)}$$

$$I = I_1 + I_2 \quad \text{--- (8)}$$

for germanium diode $n=1$

for silicon diode $n=2$

$$\text{so now } \rightarrow I = I_0 (e^{V_D/V_T} - 1) \quad \text{--- (7u)}$$

$$\rightarrow I_1 = I_0 (e^{V_D/V_T} - 1)$$

$$I_2 = I_0$$

$$\text{from above eqn, } I = I_0 (e^{V_D/V_T} - 1) + I_0$$

$$I = I_0 e^{V_D/V_T}$$



$$\frac{I}{I_0} = e^{V_D/V_T}$$

$$\log(I/I_0) = V/V_T \quad (\text{Taking log both the sides})$$

$$V = V_T \ln(I/I_0)$$

$$V = \frac{kT}{q} \ln(I/I_0)$$

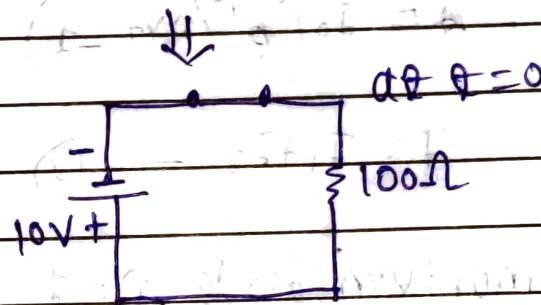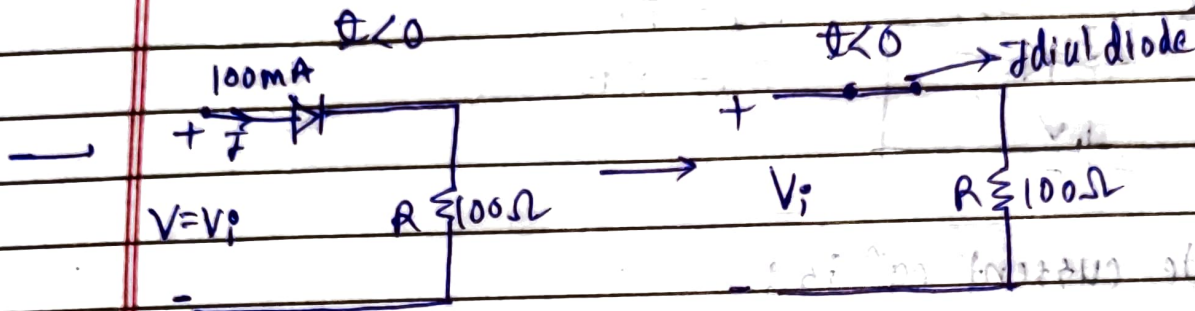- (2) A PN junction diode with a resistor of $100\ \Omega$, is FB so that a current of 100 mA flows. If the voltage across this combination is instantaneously reversed to 10 volts at $t=0$, the reverse current that flows through the diode at $t=0$, is approx.





$$I = V/R$$

$$= 10/100$$


$$= 0.1\text{ A}$$

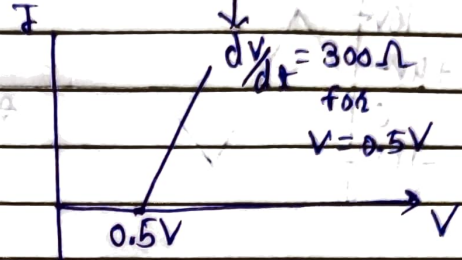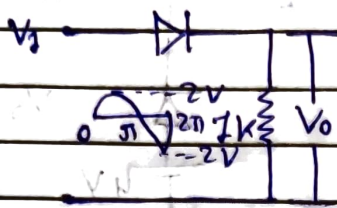- (3) Consider the circuit shown in fig(a). If the diode used here has the $V-I$ characteristic as in fig(b). Then the output waveform V_o is,




$$R_L = 300 \Omega$$



$$V_D = 0.5V$$

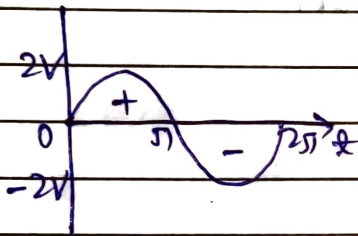

Case I

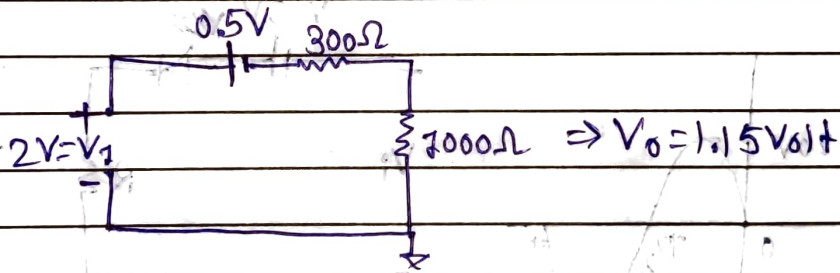


Case II $V_o = 0$

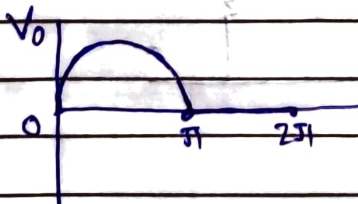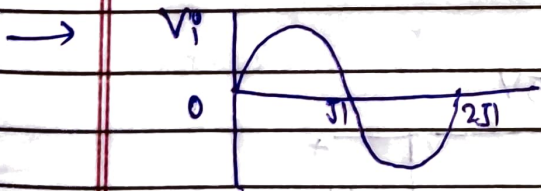


(b) determine output voltage V_o ,


Case: 1

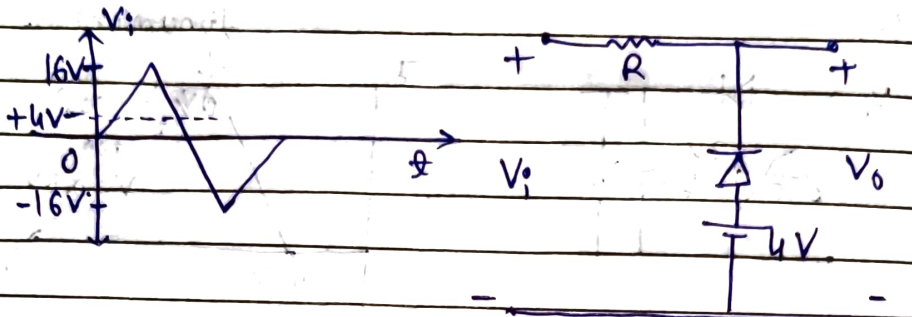

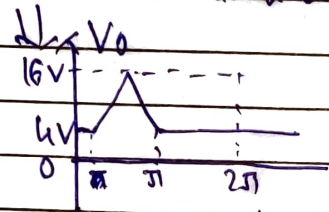
In positive cycle we'll get 16V as a output.
In negative half \Rightarrow 4V as a output,



Case: 2

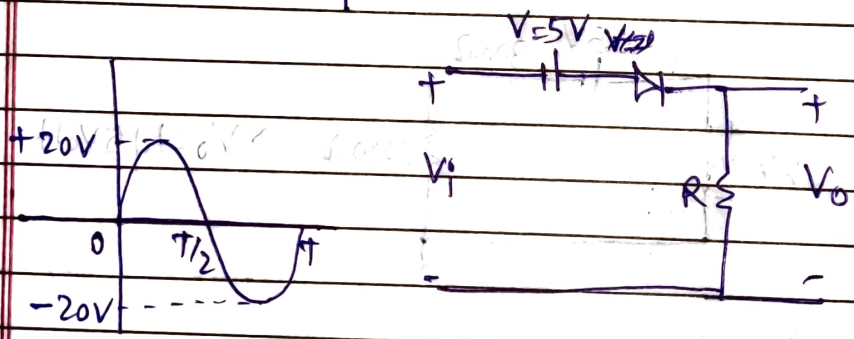


Case: 1 for +ve half cycle

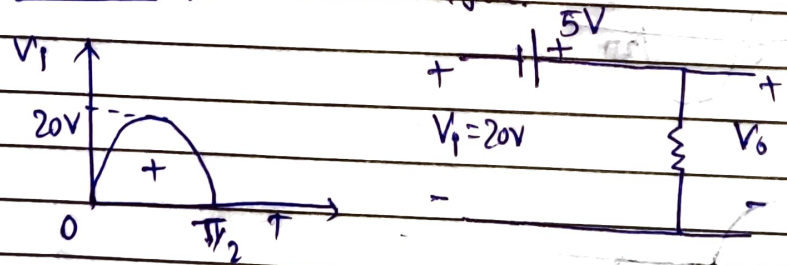


$$V_o = V_i + V = 25V$$

Case II: for -ve half cycle,

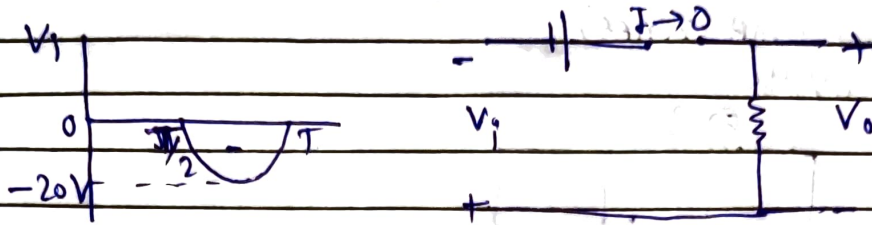

$$V_0 = 0$$

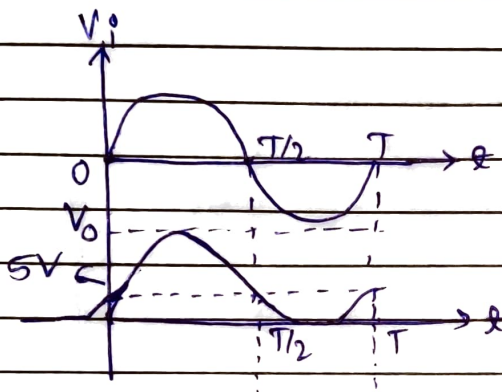

(5) $R_S = 240 \Omega$

$V_S = 30V$


$V_Z = 12V$

$R_1 = 500 \Omega$

$V_{RL} = (?)$

$V_{R_S} = (?)$

$I_Z = (?)$

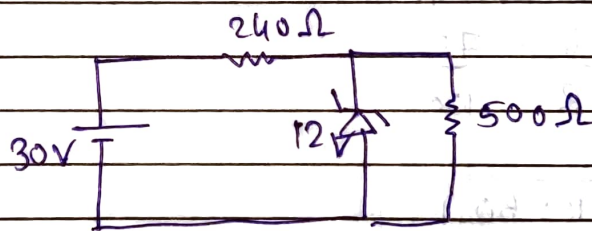

$$V_{RL} = 12V$$


$$\rightarrow I_Z = \frac{30 - 12}{240} - \frac{12}{500} = 0.099A$$

$$V_{R_S} = 18V$$

(6) $V_Z = 6V$, $R_Z = 0$

$I_{knee} = 5mA$ (Zener)

$V_R = 6V$ (Volts)

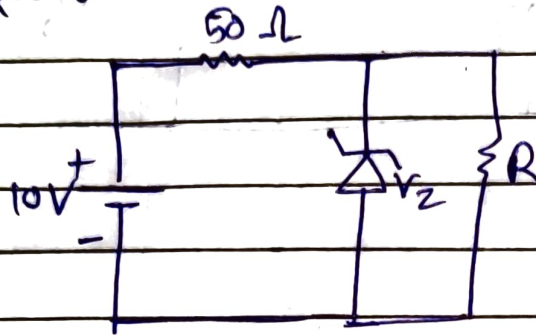

$I_Z = 5mA$


$$I_Z = \frac{10 - 6}{50} = \frac{6}{R}$$

$$\frac{5}{1000} = \frac{4}{50} - \frac{6}{R}$$

$$\frac{6}{R} = \frac{80 - 5}{1000}$$

$$\frac{6}{R} = \frac{75}{1000}$$

$$R = 80 \Omega$$

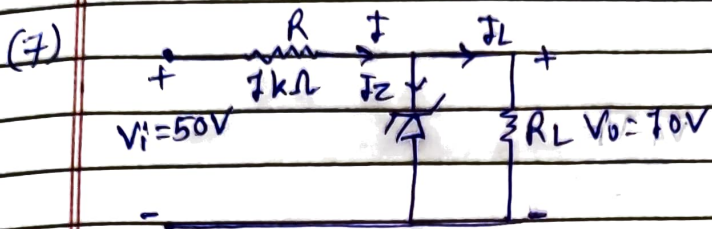

→ $V_o = 10V$ hence $V_z = 10V$

$$I = \frac{50-10}{R} = \frac{40}{1000} = 40mA$$

Using KCL, $I = I_z + I_L$

$$40 = I_z + I_L$$

→ Range of $I_L \Rightarrow 0$ to $40mA$.

for R_L ,

$$R_L = V_o / I_L = 10 / I_L$$

for $I_L = 0 \Rightarrow R_L = \infty$

$$I_L = 40 \Rightarrow R_L = 10 / 40 \times 10^3 = 250\Omega$$

→ Max power across zener diode = $V_z (I_z)_{max}$

→ $V_z = 10V$, $I_z + I_L = 40 \Rightarrow (I_L)_{max} = 40mA$

$$\therefore \text{Max Power} = V_z (I_z)_{max} \\ = (10)(40) \times 10^{-3}$$

$$= 0.4 \text{ watt}$$