



Activity



Chat



Teams



Assignments



Calendar



Calls




Files


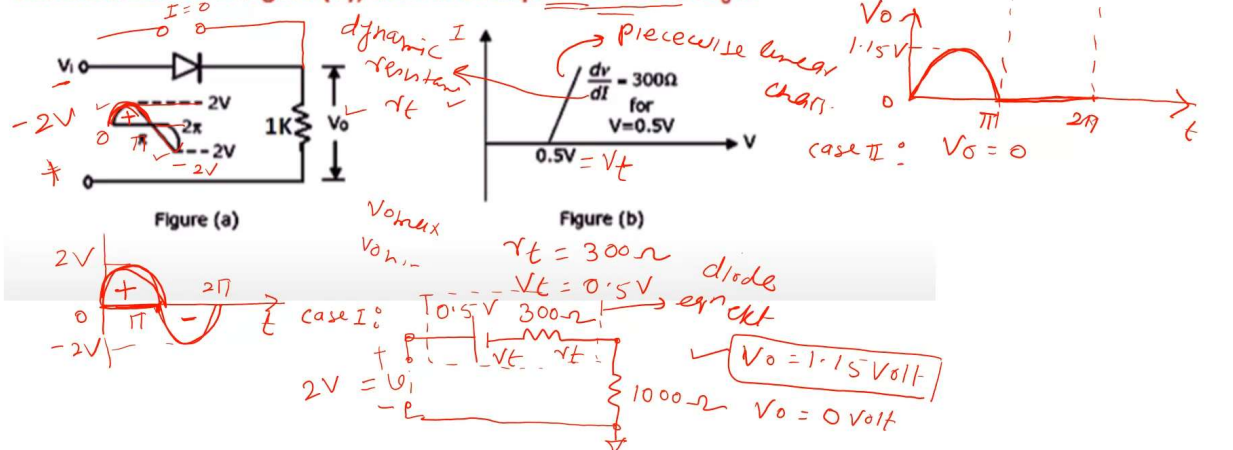
### Problem 3:

Consider the circuit shown in figure (a). If the diode used here has the V-I characteristic as in figure (b), then the output waveform  $V_o$  is



Apps



Help

41:17

L4 ECED ECED



SM



LE