

## DELD Practice Sheet - 1

B110 Krishna Pandey  
U20CS110

①

$$V_{FB} = 0.4V$$

$$I_0 = 1.17 \text{ nA} \quad (\text{reverse saturation current})$$

$$V_t = 25.2 \text{ mV}$$

$$n = 1$$

$$I_{FB} = ?$$

$$I_{FB} = I_0 \left( e^{V_{FB}/nV_t} - 1 \right)$$

$$= 1.17 \times 10^{-9} \left[ e^{0.4/25.3 \times 10^{-3}} - 1 \right]$$

$$= 1.17 \times 10^{-9} \times 7.8 \times 10^6$$

$$\boxed{I_{FB} = 9.156 \text{ mA}}$$

② Given

$$V_{FB} = 0.2V$$

$$I_{FB} = 0.1 \text{ mA}$$

$$n = 1.5$$

$$T = 25^\circ\text{C} = 298 \text{ K}$$

$$I_0 = ?$$

$$\text{Thermal voltage } V_t = \frac{T(K)}{11600} = \frac{298}{11600}$$

$$V_t = 0.0257 \text{ V}$$

$$I_{FB} = I_0 \left[ e^{V_{FB}/nV_t} - 1 \right]$$

$$0.1 \times 10^{-3} = I_0 \left[ e^{0.2/1.5 \times 0.0257} - 1 \right]$$

$$10^{-4} = I_0 [178.52]$$

$$I_0 = \frac{10^{-4}}{178.52}$$

$$I_0 = 0.5016 \text{ nA}$$

③ Conc. gradient =  $\frac{dn}{dx} = 1.5 \times 10^{22} \text{ e}^-/\text{m}^4$

diffusion current density =  $-q \times D_n \times \frac{dn}{dx}$

$$= -[-1.6 \times 10^{-19}][0.00120][1.5 \times 10^{22}]$$

$$I_D = 2.88 \text{ A/m}^2$$


④ given

$\phi_m$  = work function of metal = 4.6 eV

$\phi_{Si}$  = w.f of Si = 5.02 eV


electron affinity = 4 eV

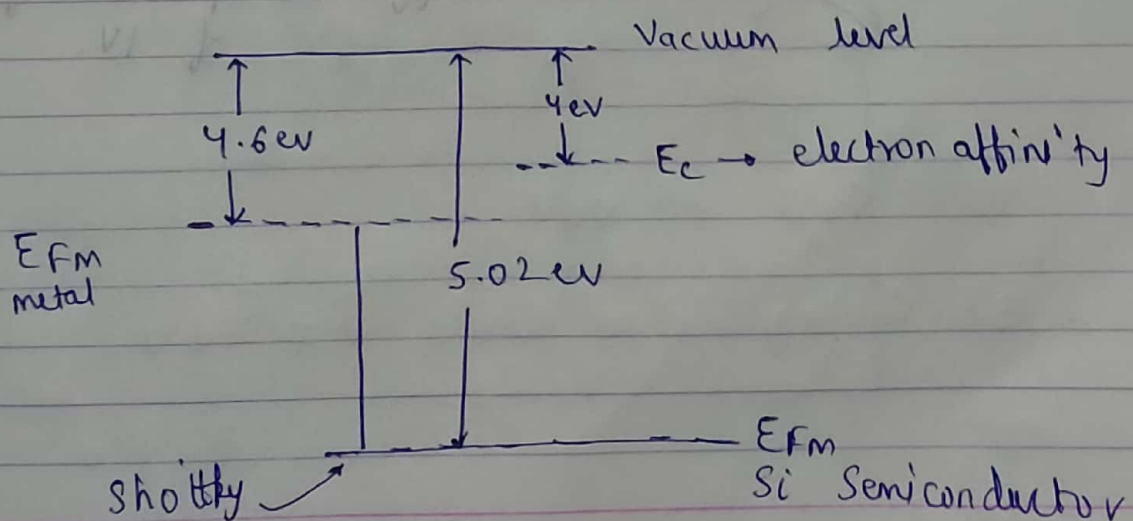⑨ The band diagram before forming the junction and under eqm condition.




⑥ It is Schottky because work function of metal is less than semi-conductor (p-type)

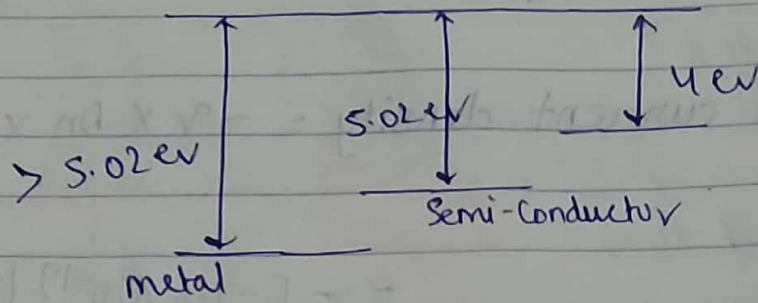
⑦ To change the contact to ohmic, the metal should have work function more than 5.02 eV



⑧

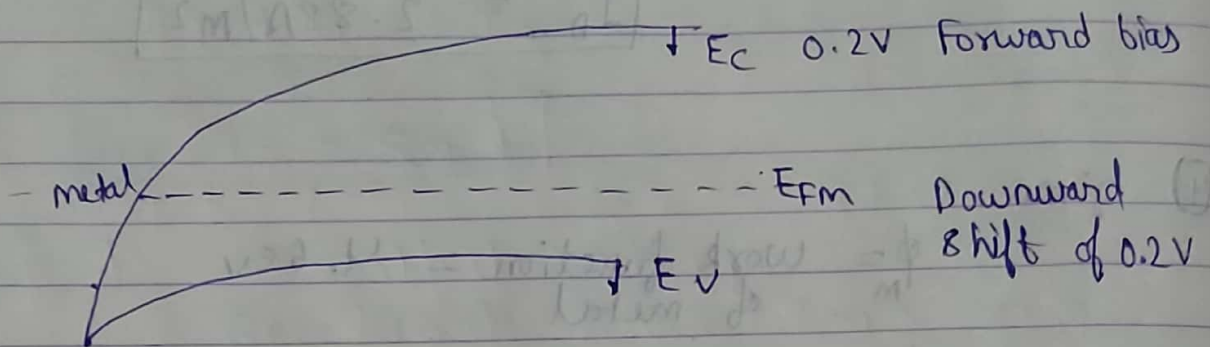


⑨

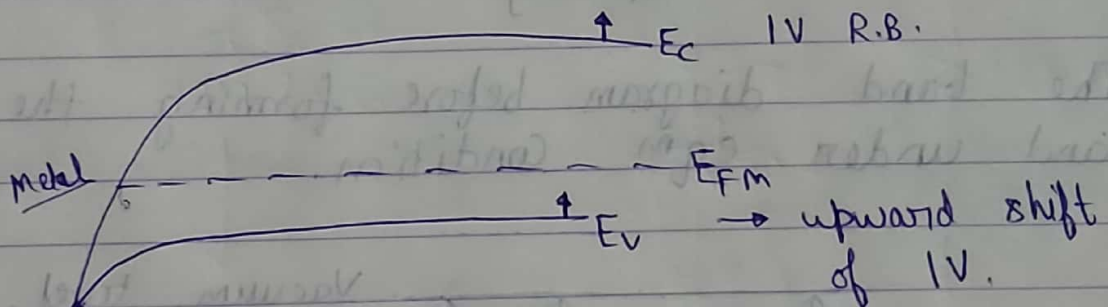



(5)

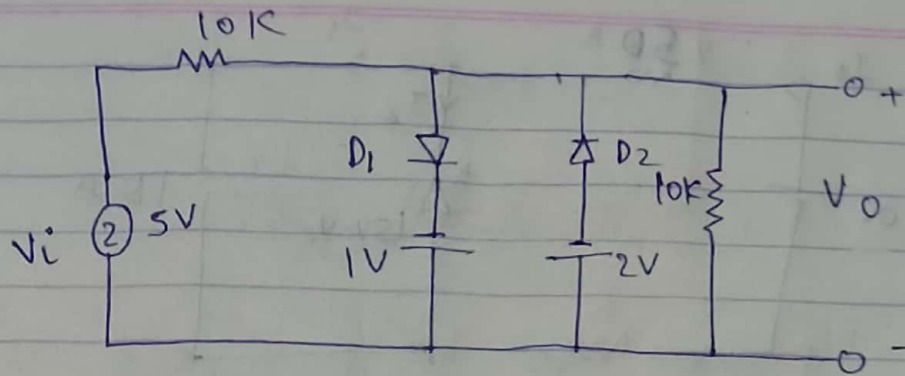

→ For output waveform,

① Positive cycle →  $V_o = -1V$


$D_1 \rightarrow FB$

$D_2 \rightarrow RB$


② Negative cycle →  $V_o = -2V$


$D_1 \rightarrow RB$

$D_2 \rightarrow FB$

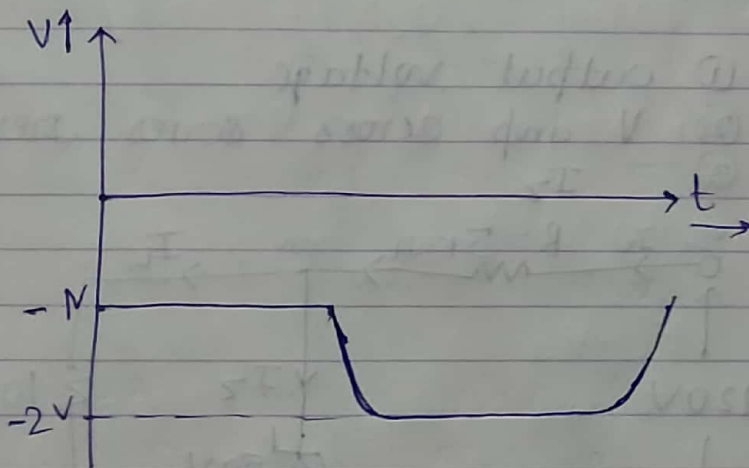

(6)

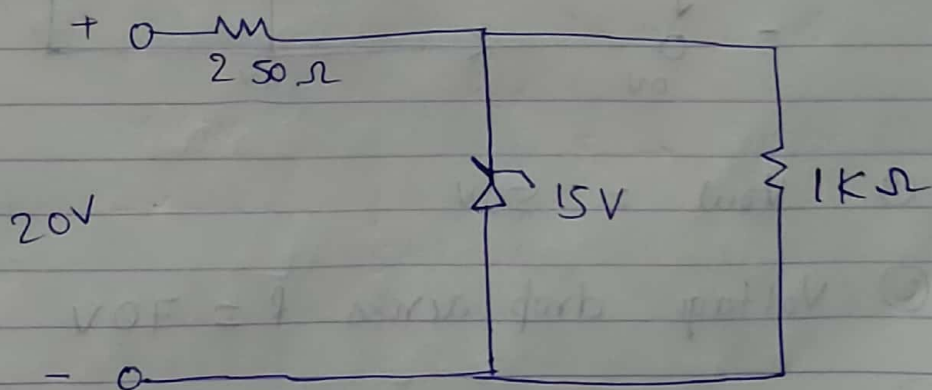

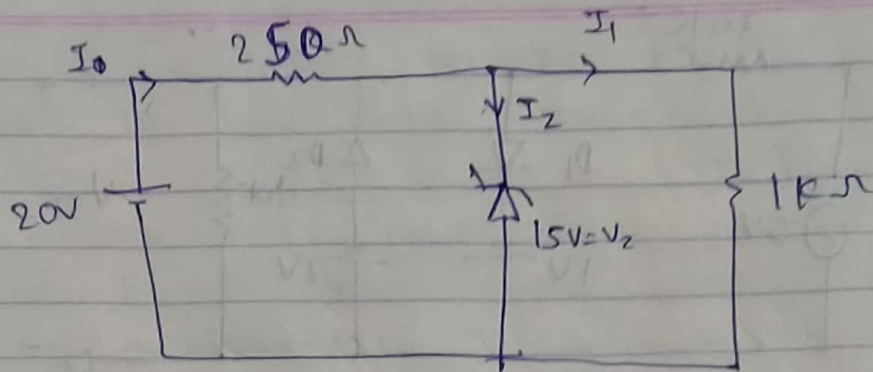


$$I_0 = \frac{20 - 15}{250} = 20 \text{ mA}$$

$$I_1 = \frac{15}{1000} = 15 \text{ mA}$$

$$I_Z + I_1 = I_0$$

$$I_Z = 5 \text{ mA}$$

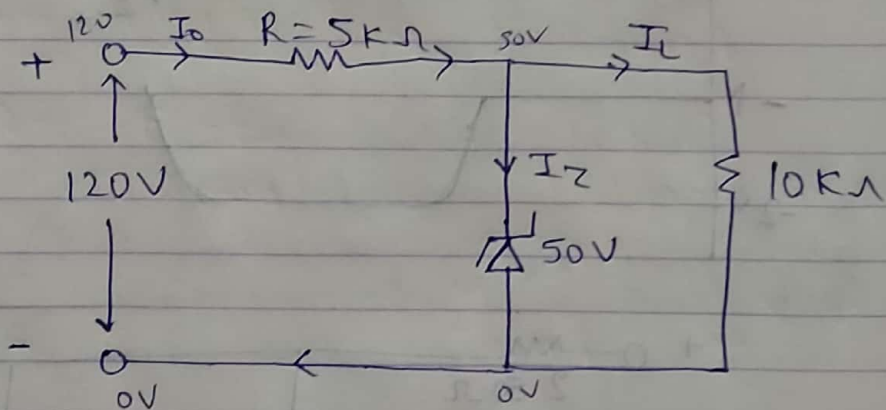- ⑦ to find
- ① output voltage
  - ② V drop across series resistor
  - ③  $I_Z$



$$① V_{out} = 50 \text{ V}$$

$$② \text{ Voltage drop across } R = 70 \text{ V}$$

③


$$I_0 = \frac{70}{5000} = 14 \text{ mA}$$

$$I_L = \frac{V_Z}{10000} = \frac{50}{10K} = 5 \text{ mA}$$

$$I_Z + I_L = I_0$$

$$I_Z = 9 \text{ mA}$$

⑧

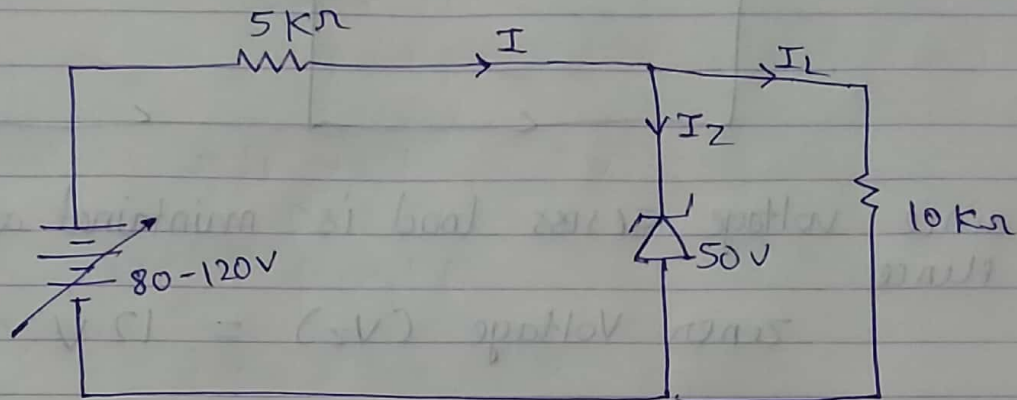

① For  $V_{out} = 80 \text{ V}$

$$I = \frac{80 - 50}{5K} = 6 \text{ mA}$$

$$I_L = \frac{50}{10K} = 5 \text{ mA}$$

$$I_Z = I - I_L = 1 \text{ mA}$$


② For  $V_{out} = 120 \text{ V}$

$$I = \frac{120 - 50}{5K} = 14 \text{ mA}$$

$$I_Z = I - I_L = 9 \text{ mA}$$

$$\therefore \begin{cases} (I_z)_{\max} = 9 \text{ mA} \\ (I_z)_{\min} = 1 \text{ mA} \end{cases}$$

⑨

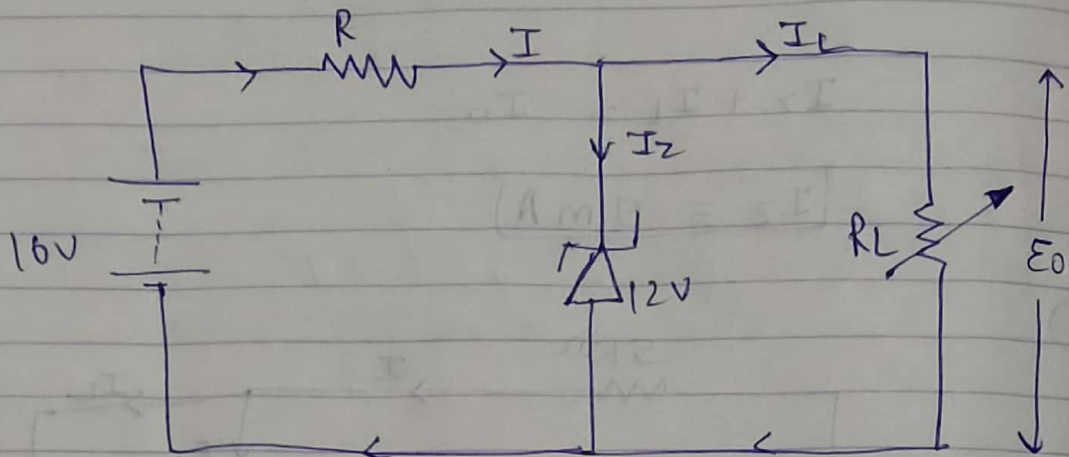

since voltage across load is maintained at 12V  
Hence

$$\text{Zener Voltage } (V_z) = 12 \text{ V}$$

$$\text{Voltage across } R = 4 \text{ V}$$

load current varies from 0 - 200 mA

$$R = \frac{E_i - E_o}{I_{z\min} + I_{\max}} = \frac{16 - 12}{(200 - 0) \text{ mA}}$$

$$= \frac{4}{200 \text{ mA}} = \frac{1}{50} \times 10^3$$

$$= 20 \Omega$$

Max. voltage rating  $> (P_z)_{\max}$

$$(P_z)_{\max} = V_z (I_z)_{\max} = 12 \times 200 \text{ mA} \\ \geq 2.4 \text{ W}$$