

Tutorial-3

Kirti Chaudhary

B073 073

- 1) $I_E = 1\text{mA}$, Collector current $I_C = 0.95\text{mA}$, calculate the base current value I_B .

Ans) $I_E = I_B + I_C$
 $I_B = I_E - I_C$
 $I_B = 1 - 0.95$
 $I_B = \underline{0.05\text{mA}}$

- 2) For a given circuit \rightarrow Current amplification is given $\alpha = 0.9$, ammeter current $= I_E = 1\text{mA}$. Calculate the value of I_B .

Ans) $I_E = 1\text{mA}$, $\alpha = 0.9$, $I_B = ?$

Relationship between α ; $I_E \rightarrow \alpha = \frac{I_C}{I_E}$

$$\rightarrow \alpha \times I_E = I_C$$

$$\rightarrow I_C = \underline{0.9\text{mA}}$$

$$\rightarrow I_E = I_B + I_C$$

$$\rightarrow I_B = I_E - I_C$$

$$\rightarrow I_B = 1 - 0.9$$

$$\rightarrow I_B = \underline{0.1\text{mA}}$$

- 3) In a CB connection, $I_C = 0.95\text{mA}$, $I_B = 0.05\text{mA}$. Find value of α .

Ans) $I_C = 0.95\text{mA}$, $I_B = 0.05\text{mA}$.

$$\rightarrow I_E = I_B + I_C$$
$$= \underline{1\text{mA}}$$

$$\rightarrow \alpha = \frac{I_c}{I_E} = \underline{0.95mA}$$

4) In a CB connection, the emitter current is $1mA$. If the emitter circuit is open, the collector current is $50\mu A$. Find the total collector current, $\alpha = 0.92$.

Ans) Given $\rightarrow I_E = 1mA$, $I_c = 0.50mA$, $\alpha = 0.92$
 $I_{CO} = ?$

$$\rightarrow I_E = I_c + I_{CO}$$

$$\rightarrow 1 = 0.50 + 0.92 \times I_{CO}$$

$$\rightarrow 0.5 = 0.92 \times I_{CO}$$

$$\rightarrow I_{CO} = \underline{0.54mA}$$

5) Find value of β if \rightarrow

(i) $\alpha = 0.9$

$$\rightarrow \beta = \frac{\alpha}{1-\alpha} = \frac{0.9}{0.1} = \underline{9}$$

(ii) $\alpha = 0.98$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.98}{0.02} = \underline{49}$$

$$(iii) \alpha = 0.99$$

$$\beta = \frac{\alpha}{1-\alpha} = \underline{99}$$

$$\beta_{max} = 1.16 \alpha$$

B) In a common base connection, $\alpha = 0.95$.
 The voltage drop across $2k\Omega$ resistance which is connected in the collector is $2V$.
 Find the base current.

Ans) Voltage drop across
 $R_C = 2V$

$$\rightarrow I_C = 2V / 2k\Omega = 1mA$$

$$\rightarrow \alpha = \frac{I_C}{I_E} \Rightarrow I_E = \frac{I_C}{\alpha}$$

$$\rightarrow I_E = \frac{1}{0.95} = 1.05mA$$


\rightarrow Using the relation \rightarrow

$$I_E = I_B + I_C$$

$$I_B = I_E - I_C$$

$$I_B = 1.05 - 1$$

$$I_B = 0.05mA$$

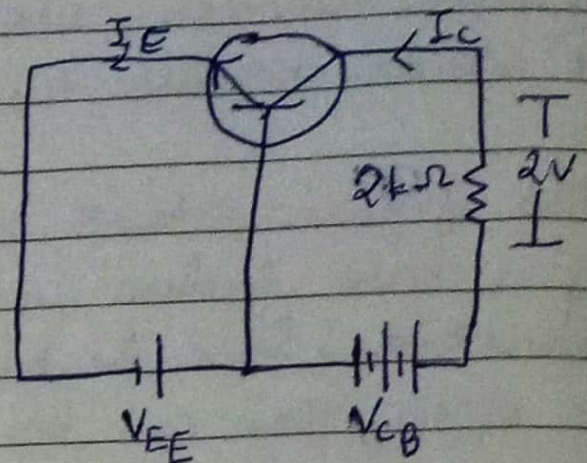

7) Calculate I_E in a transistor for which $\beta = 50$ and $I_B = 20 \mu A$.

Ans) $I_C = \beta I_B = 50 \times 20 \mu A = 1 mA$.

$\rightarrow I_E = I_C + I_B = 20 \mu A + 1 mA = \underline{1.02 mA}$

8) Find the α rating of the transistor shown in Figure below. Hence determine the value of I_C using both α and β rating of the transistor.

Ans) $I_C = \alpha I_E$, $I_C = \beta I_B$


$\rightarrow I_E = \frac{I_C}{\alpha}$

$\rightarrow I_C = I_E - I_B$
 $= 12 - 0.24$
 $= \underline{11.76 mA}$

$\alpha = \frac{I_C}{I_E} = \frac{11.76}{12} = \underline{0.98}$

$\rightarrow \beta = \frac{I_C}{I_B}$

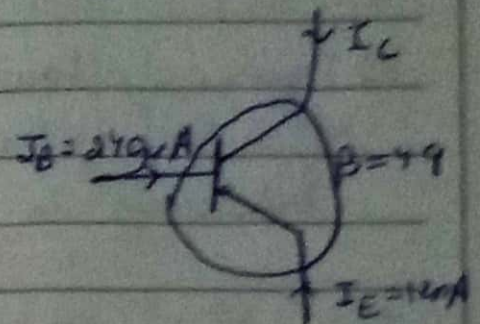$\rightarrow I_C = \beta I_B = 49 \times 0.24 = \underline{11.76 mA}$



$$I_c =$$

9) A transistor has the following ratings: $I_c(\text{max}) = 500\text{mA}$, $\beta_{\text{max}} = 300$. Determine the maximum allowable value for I_B for the device.

Ans) $I_c = 500\text{mA}$, $\beta = 300$.

$$\rightarrow \beta = \frac{I_c}{I_B}$$


$$\rightarrow I_B = \beta \times I_c$$

$$= 50 \times 10^{-3} \times 300$$

$$\rightarrow \underline{I_B = 15\text{mA}}$$

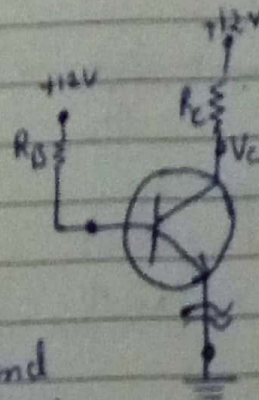
10) Figure following shows the open circuit failures in a transistor. What will be the circuit behaviour in each case.

Ans) a) This figure shows an open emitter failure in a transistor. Since the collector diode is not forward biased, it is off and there can be neither collector current nor base current.



Therefore, there will be no voltage drop across the resistor and the voltage at the base and at the collector leads to 12V.

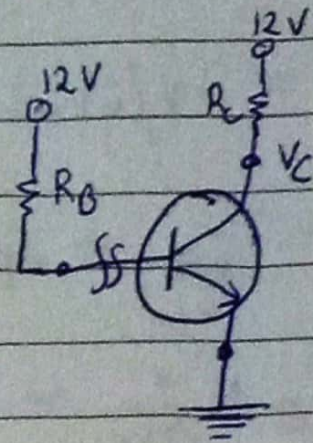b) This figure shows an open base failure in a transistor. Since the base is open, there can be no base current so that the transistor is in cut-off. Thus all the transistor current are 0A.



In case the base and collector voltage both will be 12V.

c) This figure shows an open collector failure in a transistor. In this case, the emitter diode is still ON, so we expect to see 0.7V at the base. However, we will see 12V at the collector because there is no collector current.

