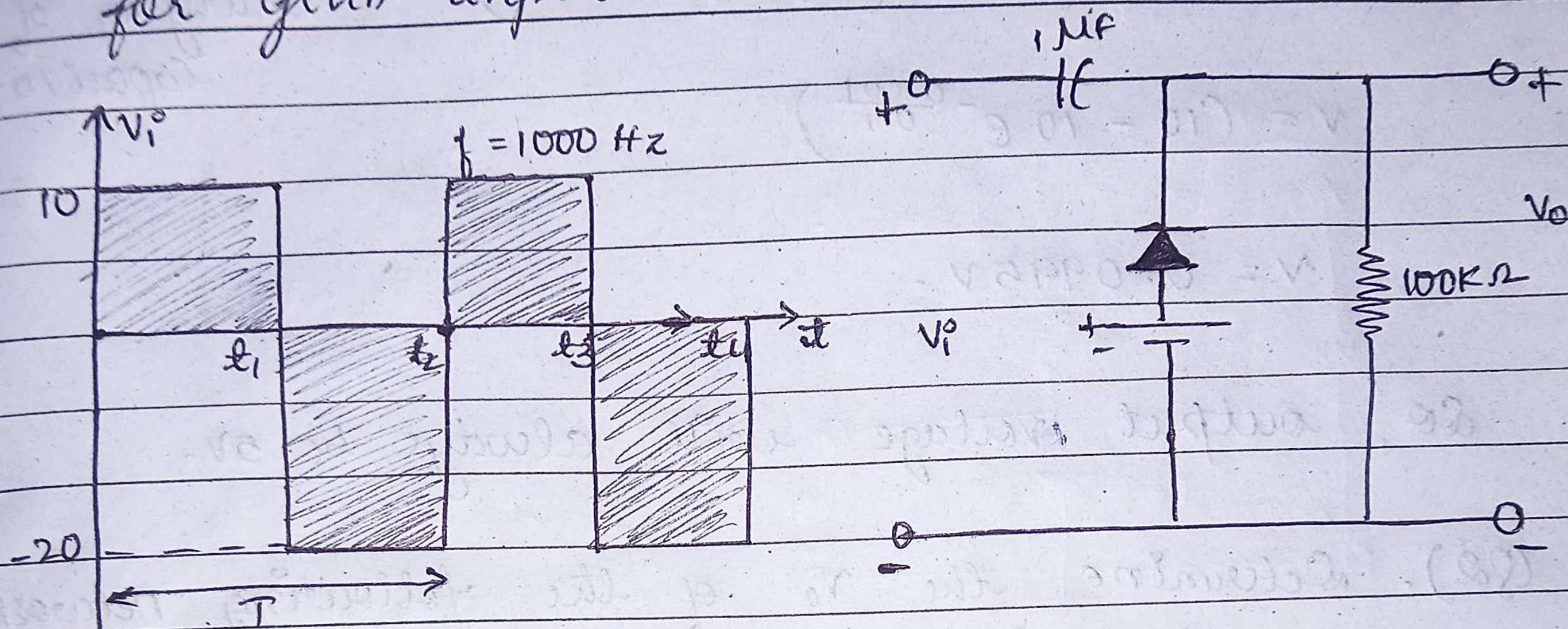


## DELD PROBLEM SHEET 2.

Q1. Determine the  $V_o$  of the following network for given input.



When input rises from  $0$  to  $10$ , means step input but output won't be like step, the capacitor charges so output will be  $5\text{V}$  until the  $V_{out}$  will be more than  $5\text{V}$ , we can calculate.

$$T = RC$$

$$= 100 \times 10^3 \times 10^{-6} = 0.1 \text{ s}$$

In  $0.1 \text{ s}$  it reaches  $63\%$  of input voltage means  $6.3 \text{ s}$ .

Given frequency  $= 1000 \text{ Hz}$

$$T = \frac{1}{1000} = 0.001 \text{ sec.}$$



→ but in 0.001 sec it will change its priority.

$$V_{out} \text{ at } 0.001 = (V_0 - V_0 e^{-t/RC})$$


charging of capacitor

$$V = (10 - 10 e^{-\frac{0.001}{0.1}})$$

$$V = 0.0995 V$$

So, output voltage will always be 5V.

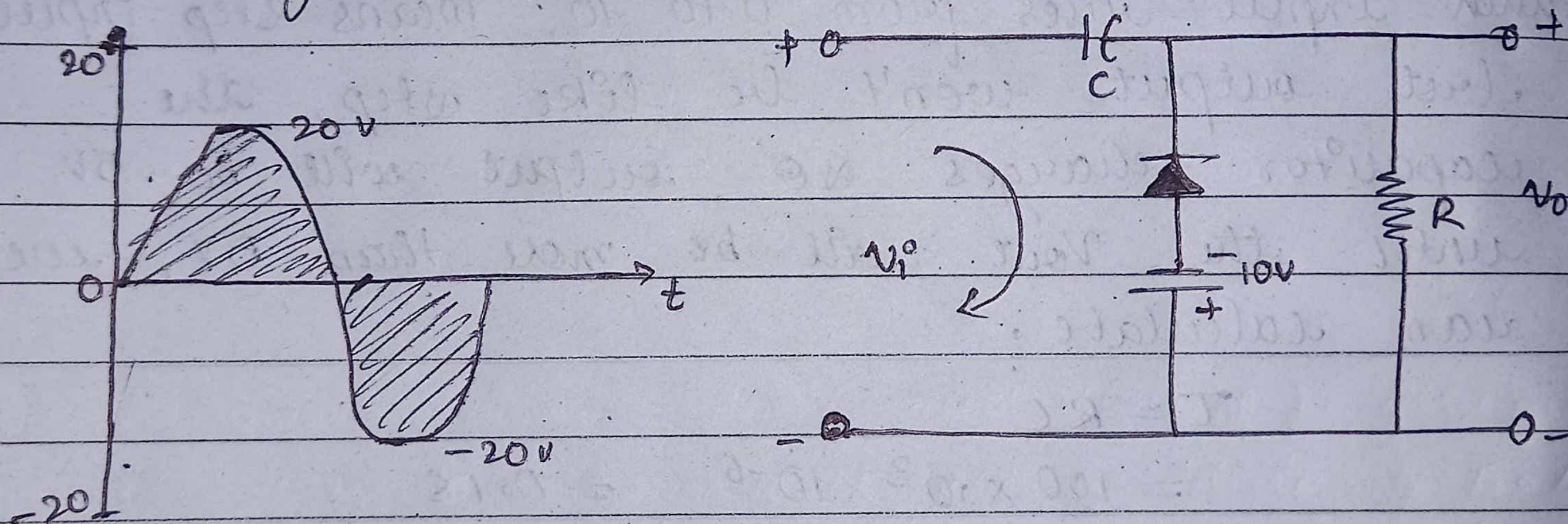Q2). Determine the  $V_o$  of the following network for given input.



$$V_{R(max)} = V_i(max) + 10 = 20V + 10V \text{ when capacitor is uncharged} \\ = 30V.$$

$$\text{So, } V_o(max) = 30$$



$$\text{Also, } V_o = V_i + 10$$

$$\text{So, } V_o(max) = +30V$$

$$V_o(min) = -10V$$



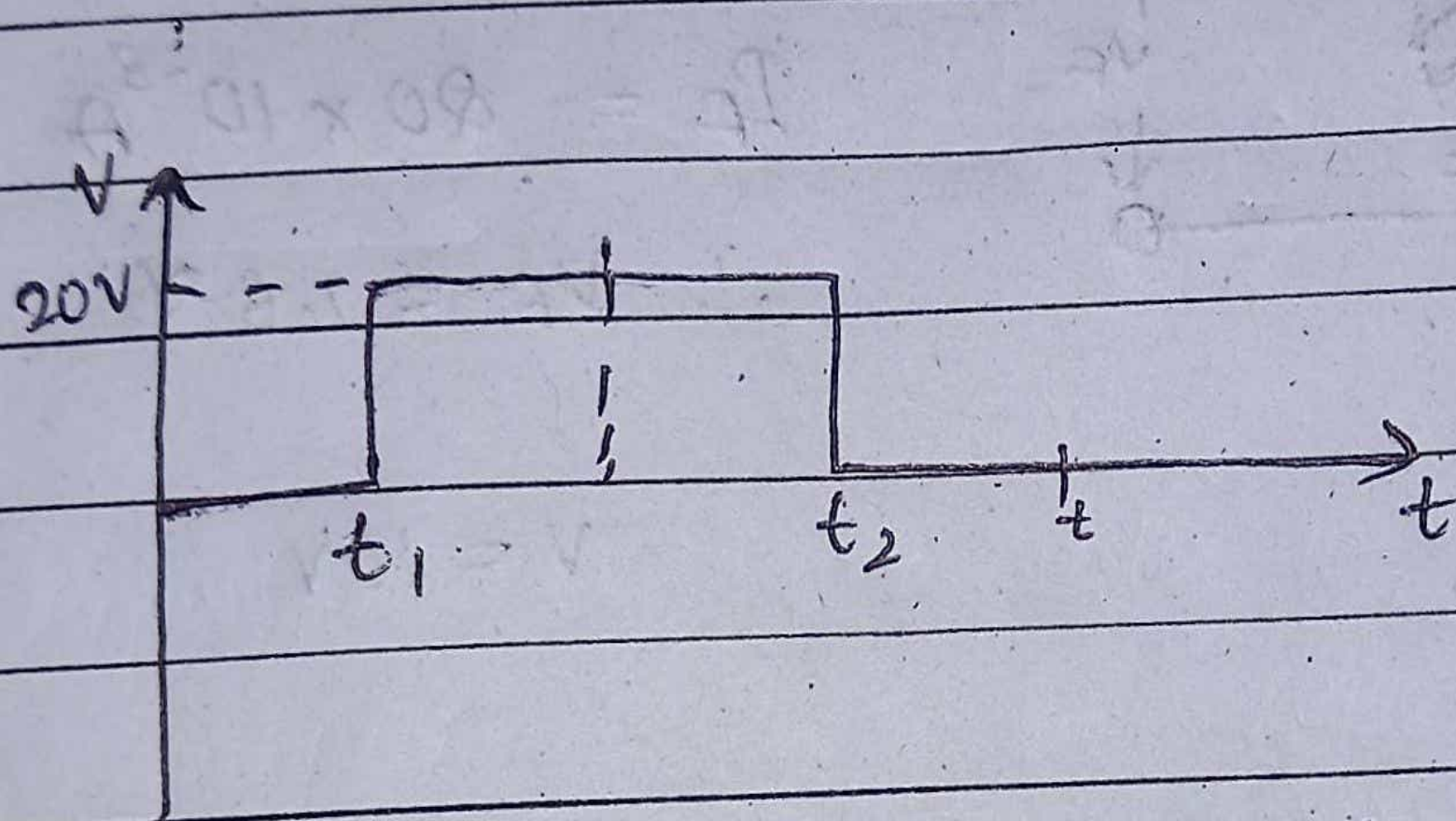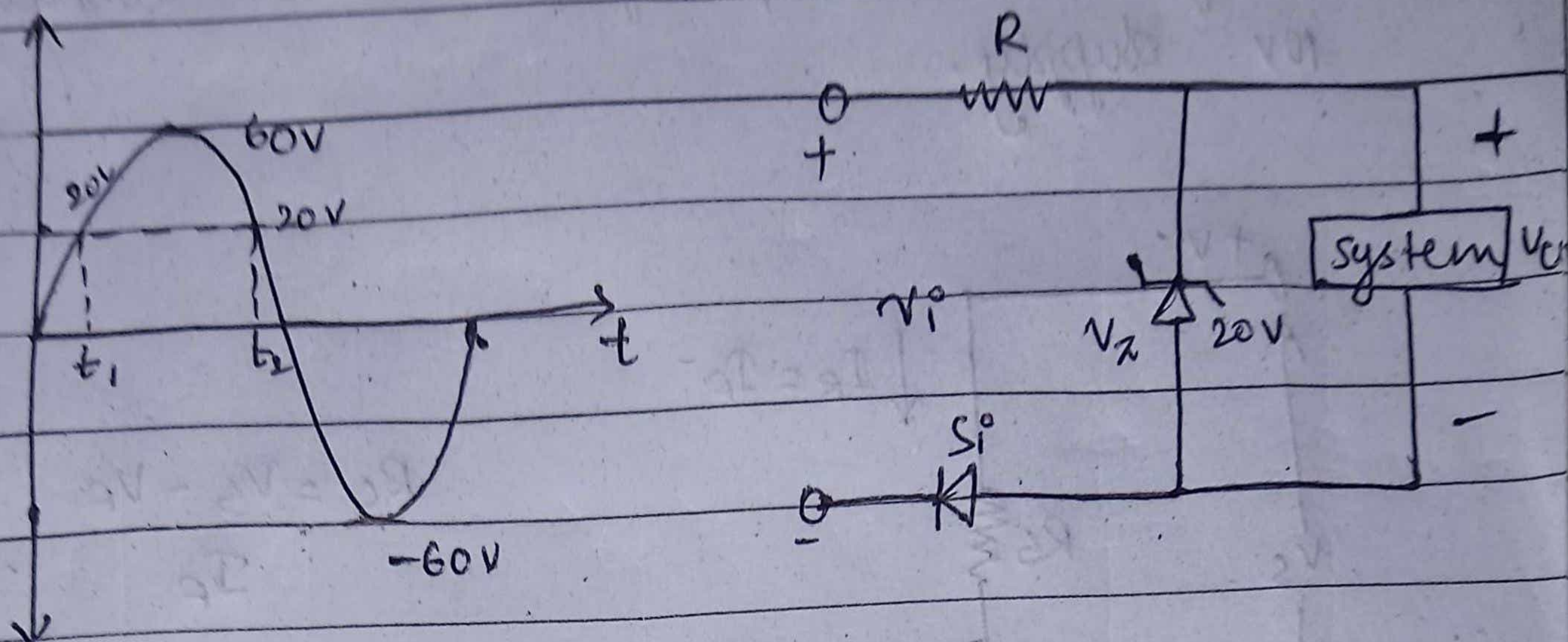Q3) Draw the output voltage waveform for the circuit.




Q4) A green colour LED emits light with the wavelength of  $5490 \text{ \AA}$ . Find the energy gap of the material used to fabricate the LED.

$$E = \frac{hc}{\lambda} = \frac{12400}{5490} \text{ eV} = 2.26 \text{ eV}$$



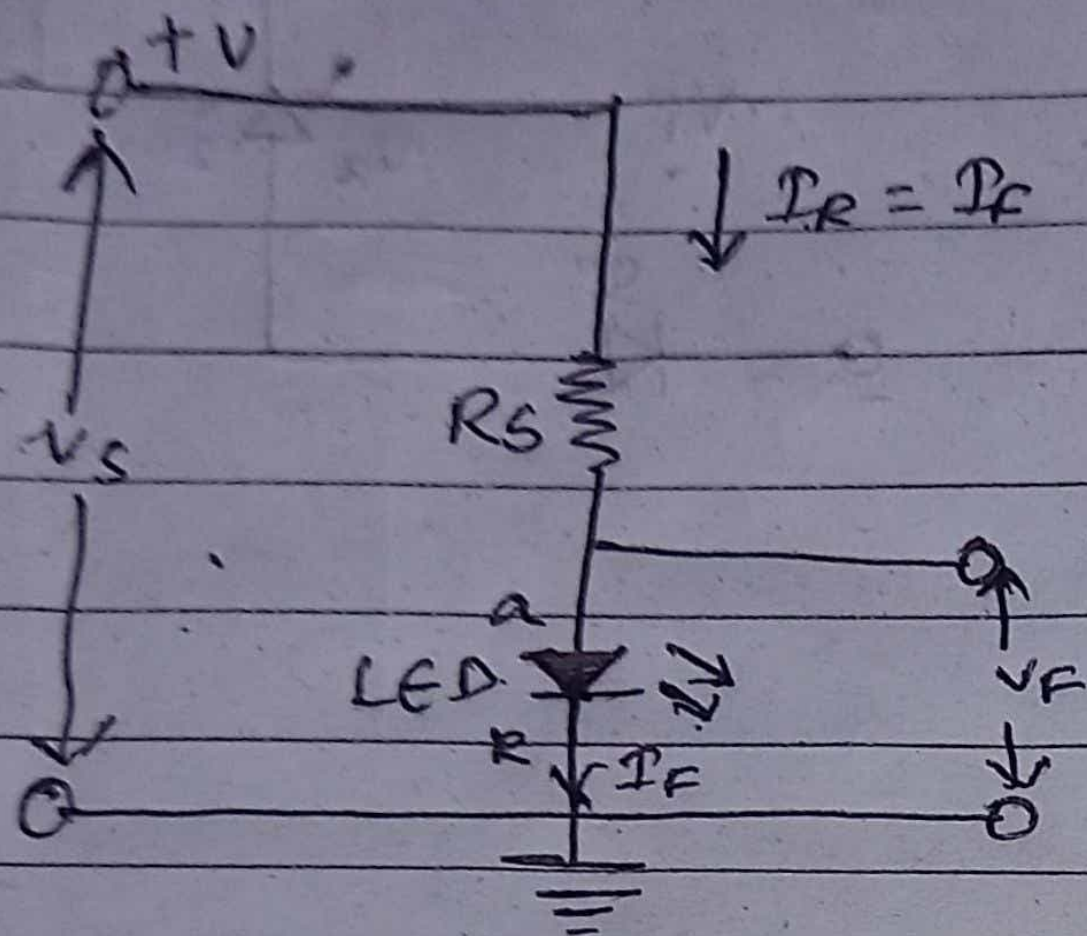Q5) Find the required series resistor to limit the current through LED to 20mA with a forward drop of 1.6V when connected to 10V supply.



$$R_s = \frac{V_s - V_F}{I_F}$$


$$I_F = 20 \times 10^{-3} \text{ A}$$

$$\therefore V_F = 1.6 \text{ V}$$

$$V = 10 \text{ V}$$

$$\therefore R_s = \frac{V_s - V_F}{I_F} = \frac{10 - 1.6}{20 \times 10^{-3}} = 420 \Omega$$

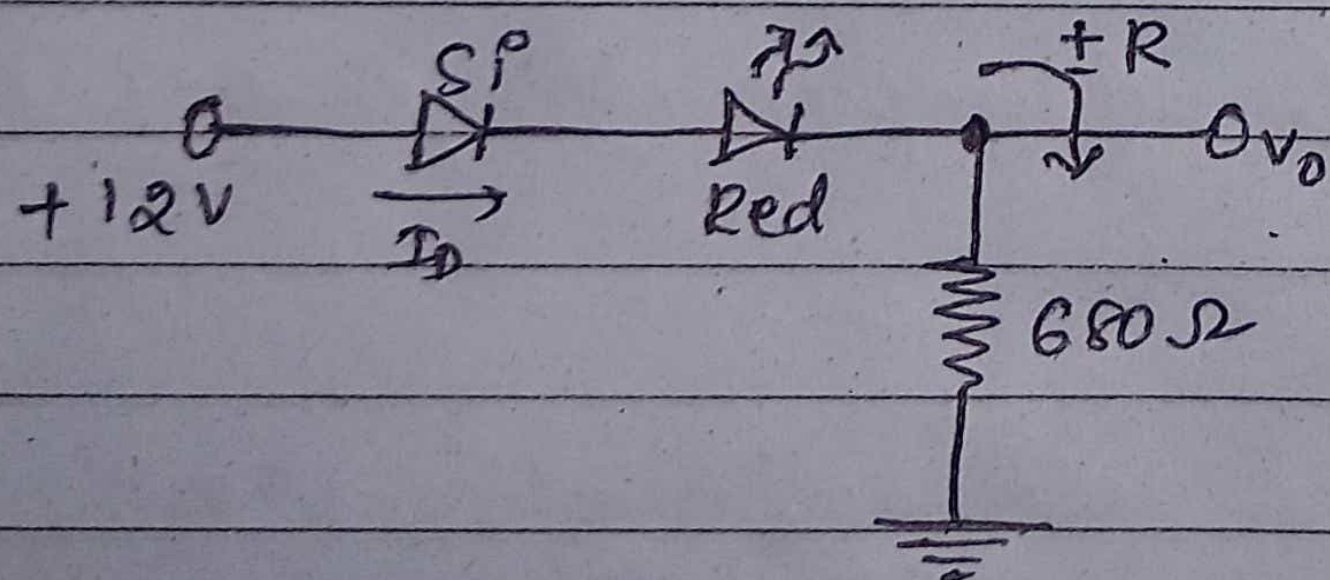Q6) Determine the  $V_o$  &  $P_D$  (Series current). Assume the forward drop across LED & diode & 1.8V and 0.7V.



$$R = \frac{V_s - V_F}{I} = \frac{12 - 2.5}{I}$$

$$\Rightarrow 680 = \frac{9.5}{I} \Rightarrow I = 0.0139 \text{ A}$$

$$V_o = IR \Rightarrow 0.0139 \times 680 = 9.5 \text{ V}$$