

## Tutorial-2

Kir H. Chaudhary

B073 0207073

1) The diffusion constant for holes in Si is  $13 \text{ cm}^2/\text{s}$ . What is the diffusion current density if the gradient hole concentration,  $\frac{dp}{dx} = -2 \times 10^{14} \text{ holes/cm}^3/\text{cm}$ ?

Ans)  $J_p = -e D_p \frac{dp}{dx}$

Given  $\Rightarrow D_p = 13 \text{ cm}^2/\text{sec}$ ,  $J_p = ?$ ,  $\frac{dp}{dx} = -2 \times 10^{14} \text{ holes/cm}^3/\text{cm}$ .

$$\Rightarrow J_p = -e D_p \frac{dp}{dx}$$

$$\Rightarrow J_p = -1.6 \times 10^{-19} \times 13 \times (-2 \times 10^{14})$$

$$\Rightarrow J_p = -41.6 \text{ mA/cm}^2$$

$$\Rightarrow J_p = -41.6 \text{ A/cm}^2$$


2) An amber coloured LED with a forward voltage drop of 2 volts is to be connected to a 5V stabilised DC power supply. Using the circuit above calculate the value of the series resistor required to limit the forward current to less than  $10 \text{ mA}$ . Also calculate the current flowing through the diode if a  $100 \Omega$  series resistor is used instead of the calculated first.

Ans)  $V_f = 2 \text{ V}$ ,  $I_{R_s} = ?$ ,  $R_s = 300 \Omega$

a)  $I_f = 10 \text{ mA}$ .

b)  $I_f = ?$ ,  $R_s = \frac{V_s - V_f}{I_f}$

$R_s = 100 \Omega$

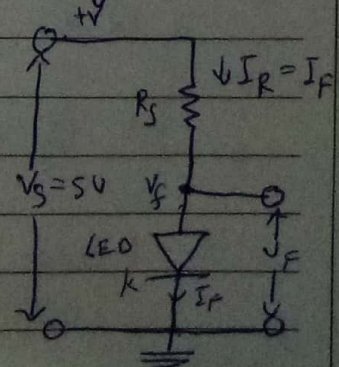



$$\rightarrow I_f = \frac{5-2}{100\Omega}$$

$$\rightarrow \underline{I_f = 0.3A}$$


3) Connecting LED's in series.

Ans)  $V_{LED}$  Using the formula

$$\rightarrow R_s = \frac{V_s - V_{LED}}{I_f}$$

$$\rightarrow V_{LED} = 3 \times 1.2V = 3 \times 1.2V = \underline{3.6V}$$

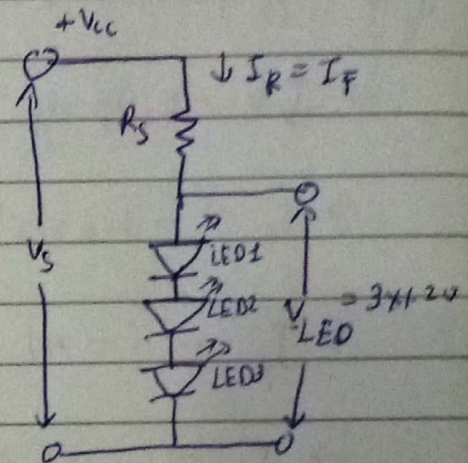
$$\rightarrow R_s = V_s - V_{LED} = 5 - 3.6 = \underline{1.4V}$$



4) Calculate the power rating for resistor RL.

Ans) given  $\rightarrow$  LED forward voltage  
 $= 3.9V = V_f$

LED forward current  
 $= 1400mA = I_f$

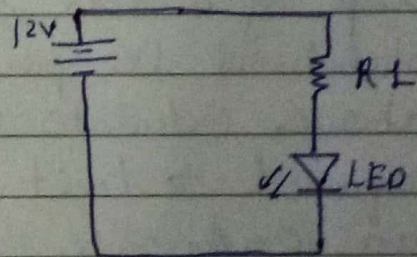

$$\rightarrow 12V - V_f - V_R = 0$$



$$\rightarrow 12V - 3.9V - V_R = 0$$

$$\rightarrow \underline{V_R = 8.1V}$$

$$\rightarrow \text{Power} = I \times V = 1.4 \times 8.1 = \underline{11.34 \text{ Watts}}$$




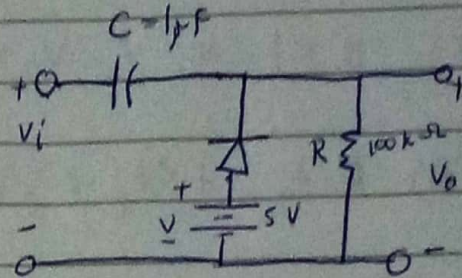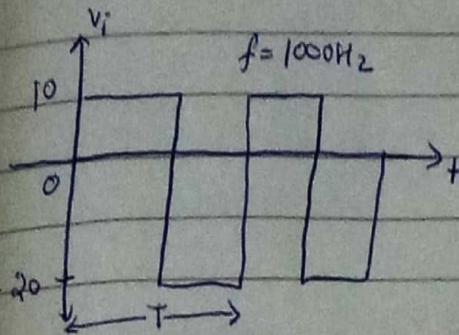5) Determine  $V_o$  for the following network with the input shown (for ideal diode).




Ans)  $T = \frac{1}{f} = \frac{1}{1000 \text{ Hz}} = 1 \text{ ms}$ ,  $t_1 = 0.5 \text{ ms}$ ,  $t_2 = 0.5 \text{ ms}$ .

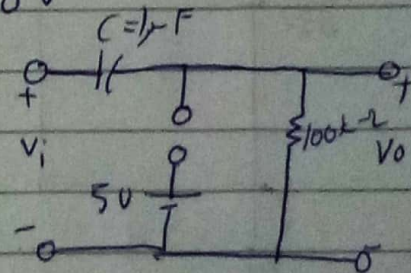a)  $V_i = 10 \text{ V} \Rightarrow 0 < t < t_1 \Rightarrow V_i = 10 \text{ V}$   
 first interval  $\Rightarrow I_o = 0 \text{ A}$ ,  $V_o = 0 \text{ V}$




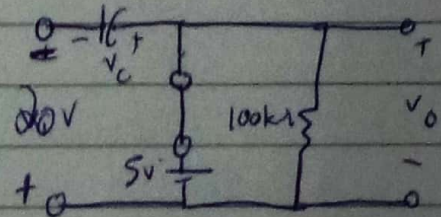b)  $V = -20 + V_C - 5 \text{ V} = 0$ ,  $V_o = 5 \text{ V}$   
 second interval  $\Rightarrow V_C = 25 \text{ V}$



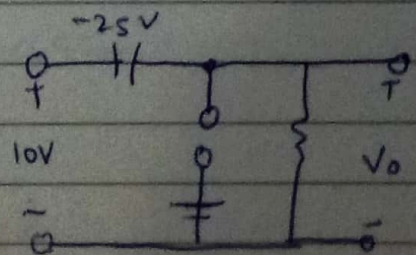c) Applying KVL to circuit.

$$\begin{aligned} \rightarrow 10 \text{ V} + 25 \text{ V} - V_o &= 0 \\ \rightarrow V_o &= 35 \text{ V} \end{aligned}$$



$\rightarrow$  Discharge at time  $t = RC$

$$\rightarrow RC = 100 \times 10^3 \times 0.1 \times 10^{-3} = 10 \text{ ms}$$



Total discharge  $= 5t \approx 5 \times 10 \text{ ms} = 50 \text{ ms}$ .

Thus the cases can be concluded that  $\rightarrow$

I)  $0 < t < t_1$  :  $V_o = 0 \text{ V}$

II)  $t_1 < t < t_2$  :  $V_o = 5 \text{ V}$

III)  $t_2 < t < t_3$  :  $V_o = 35 \text{ V}$

Thus we can plot the output as  $\rightarrow$

